



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Display Drivers](#) > APP 415

Keywords: LCDs, LCD displays, LCD drivers, triplex, duplex, opamps, operational amplifiers, op amps

#### APPLICATION NOTE 415

## Buffering Scheme Drives Large LCDs

Jul 09, 1998

*Abstract: This application notes shows how to buffer the triplex backplane drive outputs of a LCD driver such as MAX7231 family to increase the capacitive drive capability. This enables a large LCD to be driven without ghosting and other artifacts due to backplane waveform distortion.*

To conserve pins, many LCD Drivers triplex their drive signals—a technique that enables AC waveforms on three common lines and three segment lines to activate any standard character of a seven-segment display. Large LCDs of 1" or more exhibit a large capacitance between the common and segment electrodes (several nonofarads), which presents a problem for standard LCD drivers.

These drivers' high output impedance (50K $\Omega$ , for example) causes difficulty in driving capacitance, and the consequent AC-Waveform distortion can produce ghosting and shadow segments in the display. The drive circuit in **Figure 1** solves this problem by introducing a buffer amplifier for each of the three common lines. Each amplifier may be programmed independently for a quiescent current of 10, 100 or 1000 $\mu$ A. In this application, the bias network applies a voltage that sets the three quiescent currents to 100 $\mu$ A.

The display driver and triple op amp operate between 5V and ground, and the COM signals range from 5V to ~ 1V. To assure that these signals remain within the amplifiers' common-mode range. We attenuate the signals by one half and operate the buffers at a gain of two. The circuit drives eight 1" displays and is suitable for ambient temperature variations of 15°F or less. At the highest expected temperature, you should adjust R<sub>1</sub> so that no "off" segments are visible.

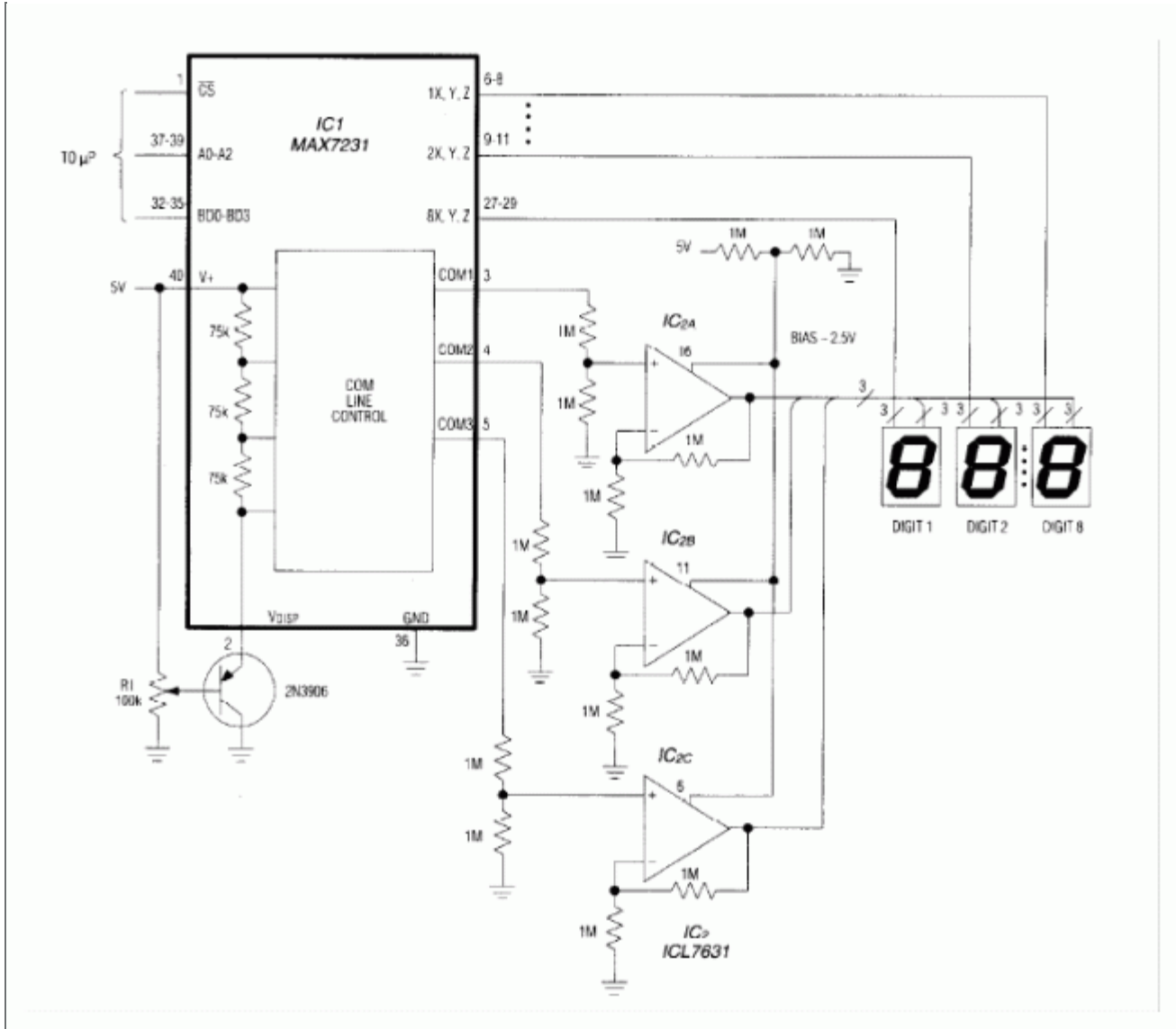


Figure 1. Three buffer amplifiers enable this standard LCD driver (IC1) to control eight large (1") seven-segment displays."

Related Parts		
<a href="#">MAX7231</a>	8-Digit, Triplexed LCD Decoder Driver	<a href="#">Free Samples</a>
<a href="#">MAX7232</a>	8-Digit, Triplexed LCD Decoder Driver	<a href="#">Free Samples</a>
<a href="#">MAX7233</a>	8-Digit, Triplexed LCD Decoder Driver	<a href="#">Free Samples</a>
<a href="#">MAX7234</a>	8-Digit, Triplexed LCD Decoder Driver	<a href="#">Free Samples</a>

**More Information**

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

---

Application Note 415: <http://www.maximintegrated.com/an415>

APPLICATION NOTE 415, AN415, AN 415, APP415, Appnote415, Appnote 415

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>